

LASERWOLF


FX TYPE: Multi FX


© madbeanpedals

2015 edition

Previous Version: http://www.madbeanpedals.com/projects/Laserwolf/Laserwolf_2014.pdf

5.2"W x 3.225"H

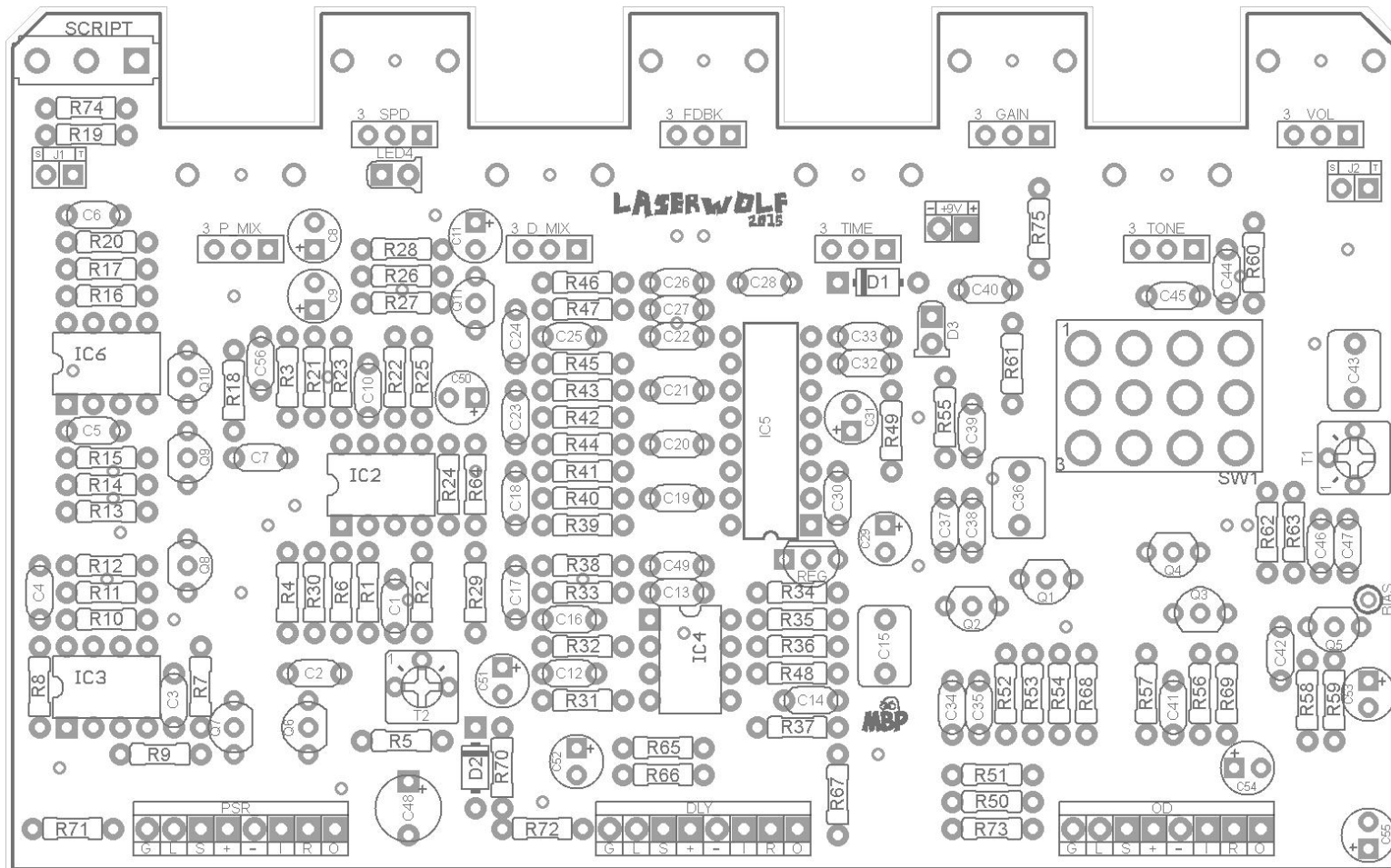

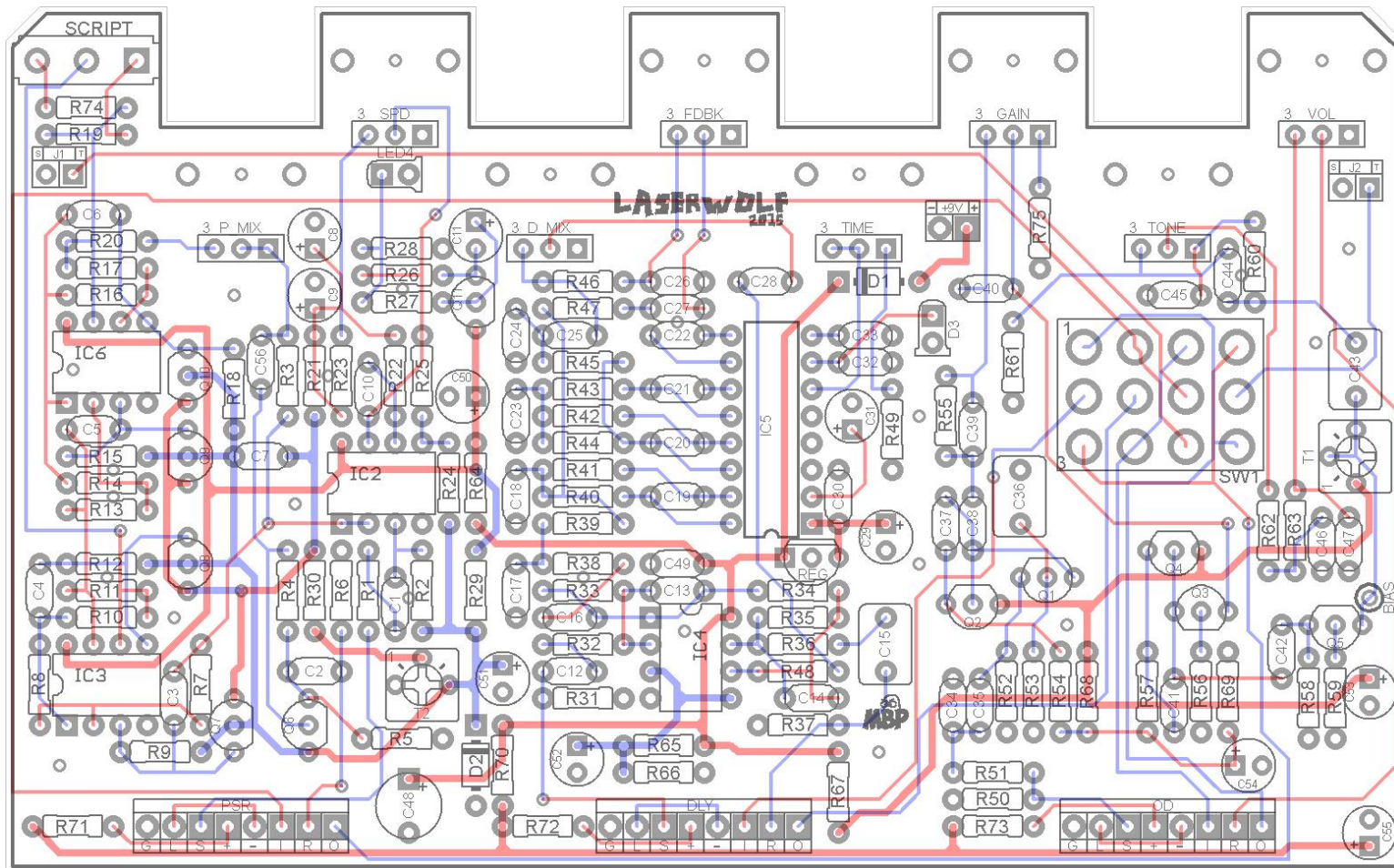

You can download the Photoshop template used for the drilling guide here:
www.madbeanpedals.com/projects/Laserwolf/Laserwolf_DRILL.zip


| B.O.M. | | | | | | | | | |
|-----------|------|-----------|------|------|-------|-------------|------------|-----------|---------|
| Resistors | | Resistors | | Caps | | Caps | | IC | |
| R1 | 10k | R39 | 10k | C1 | 10n | C39 | 470pF | IC2 | TL072 |
| R2 | 470k | R40 | 10k | C2 | 47n | C40 | 150pF | IC3 | TL072 |
| R3 | 150k | R41 | 10k | C3 | 47n | C41 | 100n | IC4 | TL072 |
| R4 | 150k | R42 | 10k | C4 | 47n | C42 | 22n | IC5 | PT2399 |
| R5 | 56k | R43 | 10k | C5 | 47n | C43 | 1uF | IC6 | TL072 |
| R6 | 150k | R44 | 20k | C6 | 47n | C44 | 10n | Regulator | |
| R7 | 10k | R45 | 1k | C7 | 47n | C45 | 10n | REG | LM78L05 |
| R8 | 10k | R46 | 1k | C8 | 10uF | C46 | 1n | Switches | |
| R9 | 22k | R47 | 12k | C9 | 4u7 | C47 | 2n2 | SW1 | 4PDT |
| R10 | 10k | R48 | 12k | C10 | 10n | C48 | 470uF | SCRIPT | SPDT |
| R11 | 10k | R49 | 1k5 | C11 | 1uF | C49 | 100n | Trimmers | |
| R12 | 22k | R50 | 1M | C12 | 100n | C50 | 10uF | T1 | 100k |
| R13 | 10k | R51 | 470R | C13 | 10pF | C51 | 22uF | T2 | 250k |
| R14 | 10k | R52 | 1M | C14 | 100pF | C52 | 10uF | Pots | |
| R15 | 22k | R53 | 10k | C15 | 1uF | C53 | 10uF | TONE | 100kA |
| R16 | 10k | R54 | 10M | C16 | 100n | C54 | 10uF | VOL | 100kA |
| R17 | 10k | R55 | 470k | C17 | 4n7 | C55 | 10uF | P_MIX | 100kB |
| R18 | 22k | R56 | 10k | C18 | 4n7 | C56 | 100n | TIME | 25kB |
| R19 | 24k | R57 | 10M | C19 | 2n2 | Diodes | | GAIN | 500kA |
| R20 | 68k | R58 | 82k | C20 | 2n2 | D1 | 1N5817 | SPD | 500kC |
| R21 | 3M9 | R59 | 4k7 | C21 | 100n | D2 | 5.1v Zener | D_MIX | 50kB |
| R22 | 150k | R60 | 47k | C22 | 100n | D3 | GREEN 5MM | FDBK | 50kB |
| R23 | 4k7 | R61 | 82k | C23 | 4n7 | Transistors | | | |
| R24 | 150k | R62 | 10k | C24 | 47n | Q1 | 2N5457 | | |
| R25 | 470k | R63 | 10k | C25 | 220n | Q2 | 2N5457 | | |
| R26 | 1M | R64 | 22R | C26 | 47n | Q3 | 2N5457 | | |
| R27 | 1k | R65 | 100k | C27 | 22n | Q4 | 2N5457 | | |
| R28 | 560R | R66 | 100k | C28 | 220n | Q5 | J201 | | |
| R29 | 10k | R67 | 22R | C29 | 10uF | Q6 | 2N5087 | | |
| R30 | 1M | R68 | 10k | C30 | 100n | Q7 | 2N5457 | | |
| R31 | 1M | R69 | 10k | C31 | 47uF | Q8 | 2N5457 | | |
| R32 | 470k | R70 | 330R | C32 | 100n | Q9 | 2N5457 | | |
| R33 | 470k | R71 | 4k7 | C33 | 100n | Q10 | 2N5457 | | |
| R34 | 22k | R72 | 4k7 | C34 | 220pF | Q11 | J112 | | |
| R35 | 20k | R73 | 4k7 | C35 | 22n | | | | |
| R36 | 470R | R74 | 18k | C36 | 1uF | | | | |
| R37 | 100k | R75 | 2k2 | C37 | 56n | | | | |
| R38 | 10k | | | C38 | 22n | | | | |

| Shopping List | | | | | | | |
|---------------|-----|---------------------|---------|---------|-----|----------------------|---------|
| Value | QTY | Type | Rating | Value | QTY | Type | Rating |
| 22R | 2 | Metal / Carbon Film | 1/4 W | 1n | 1 | Film | 16v min |
| 330R | 1 | Metal / Carbon Film | 1/4 W | 2n2 | 3 | Film | 16v min |
| 470R | 2 | Metal / Carbon Film | 1/4 W | 4n7 | 3 | Film | 16v min |
| 560R | 1 | Metal / Carbon Film | 1/4 W | 10n | 4 | Film | 16v min |
| 1k | 3 | Metal / Carbon Film | 1/4 W | 22n | 4 | Film | 16v min |
| 1k5 | 1 | Metal / Carbon Film | 1/4 W | 47n | 8 | Film | 16v min |
| 2k2 | 1 | Metal / Carbon Film | 1/4 W | 56n | 1 | Film | 16v min |
| 4k7 | 5 | Metal / Carbon Film | 1/4 W | 100n | 10 | Film | 16v min |
| 10k | 22 | Metal / Carbon Film | 1/4 W | 220n | 2 | Film | 16v min |
| 12k | 2 | Metal / Carbon Film | 1/4 W | 1uF | 3 | Film | 16v min |
| 18k | 1 | Metal / Carbon Film | 1/4 W | 1uF | 1 | Electrolytic | 16v min |
| 20k | 2 | Metal / Carbon Film | 1/4 W | 4u7 | 1 | Electrolytic | 16v min |
| 22k | 5 | Metal / Carbon Film | 1/4 W | 10uF | 7 | Electrolytic | 16v min |
| 24k | 1 | Metal / Carbon Film | 1/4 W | 22uF | 1 | Electrolytic | 16v min |
| 47k | 1 | Metal / Carbon Film | 1/4 W | 47uF | 1 | Electrolytic | 16v min |
| 56k | 1 | Metal / Carbon Film | 1/4 W | 470uF | 1 | Electrolytic | 16v min |
| 68k | 1 | Metal / Carbon Film | 1/4 W | TL072 | 4 | | |
| 82k | 2 | Metal / Carbon Film | 1/4 W | PT2399 | 1 | | |
| 100k | 3 | Metal / Carbon Film | 1/4 W | LM78L05 | 1 | T0-92 | |
| 150k | 5 | Metal / Carbon Film | 1/4 W | 1N5817 | 1 | | |
| 470k | 5 | Metal / Carbon Film | 1/4 W | 5.1v | 1 | Zener | |
| 1M | 5 | Metal / Carbon Film | 1/4 W | LED | 1 | Green Diffused | 5mm |
| 3M9 | 1 | Metal / Carbon Film | 1/4 W | 4PDT | 1 | Solder Lug | |
| 10M | 2 | Metal / Carbon Film | 1/4 W | SPDT | 1 | On/Off/On PCB Mount | |
| 10pF | 1 | Ceramic | 16v min | 100k | 1 | Bourns 3362P | |
| 100pF | 1 | Ceramic | 16v min | 250k | 1 | Bourns 3362P | |
| 150pF | 1 | Ceramic | 16v min | 100kB | 1 | PC Mount Right Angle | 9mm |
| 220pF | 1 | Ceramic | 16v min | 25kB | 1 | PC Mount Right Angle | 9mm |
| 470pF | 1 | Ceramic | 16v min | 100kA | 2 | PC Mount Right Angle | 9mm |
| | | | | 50kB | 2 | PC Mount Right Angle | 9mm |
| | | | | 500kA | 1 | PC Mount Right Angle | 9mm |
| | | | | 500kC | 1 | PC Mount Right Angle | 9mm |


- Q7 – Q10 (2N5457) must be matched for the phaser section.
- You can sub a 2n5457 for the J112 transistor. This is only for the Phaser LFO indicator and is not essential to the operation of the circuit.

LASERWOLF


2015 ed. (c) madbeanpedals

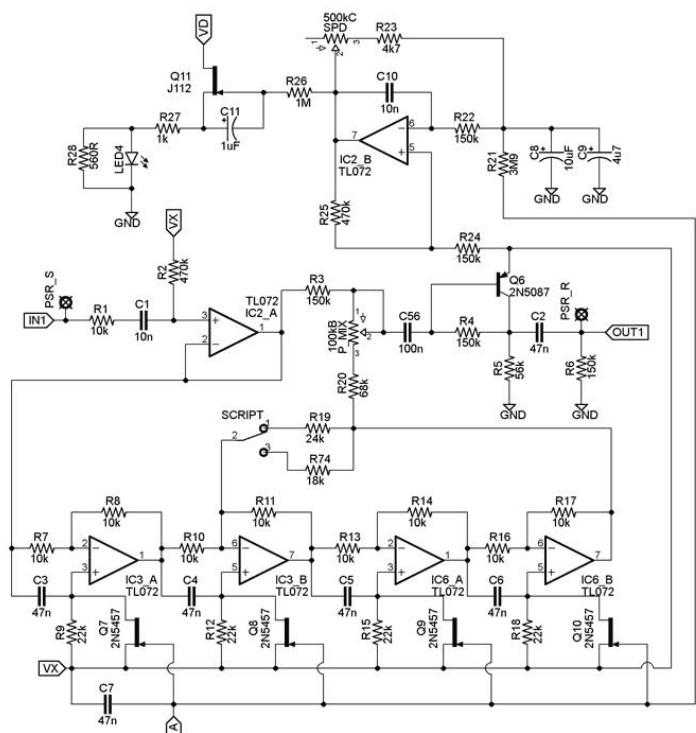




PHASER

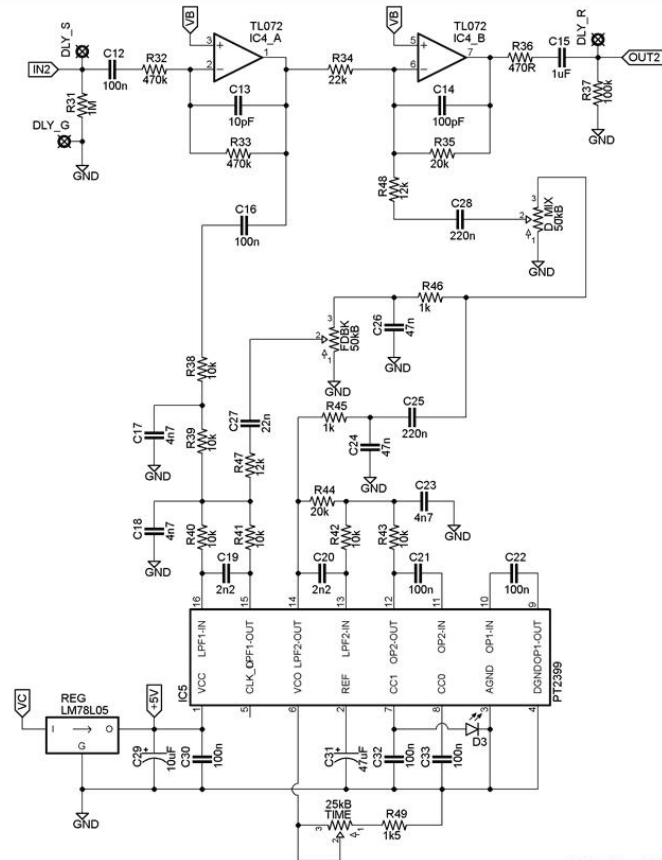


DELAY

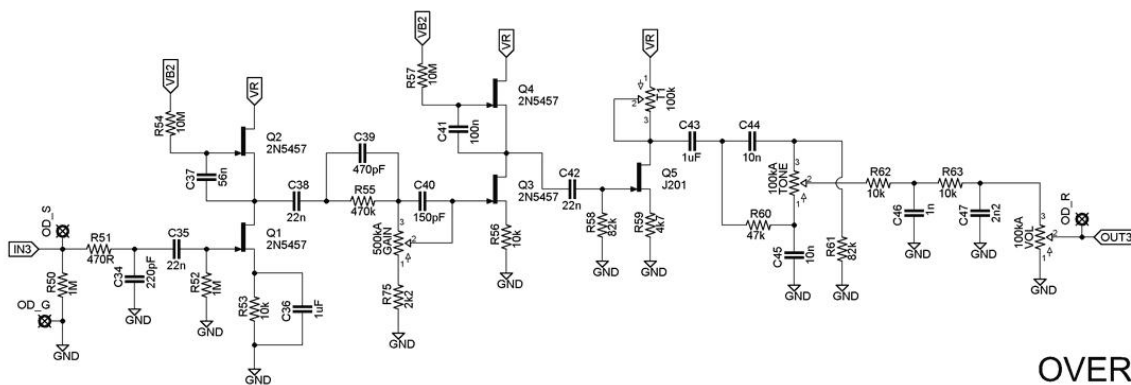

OVERDRIVE

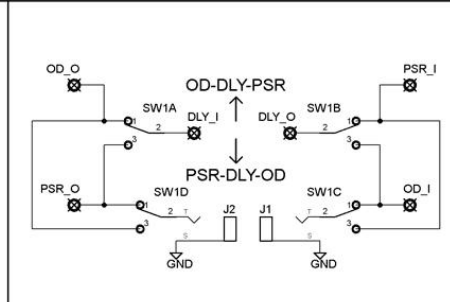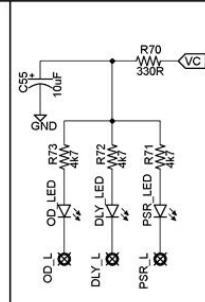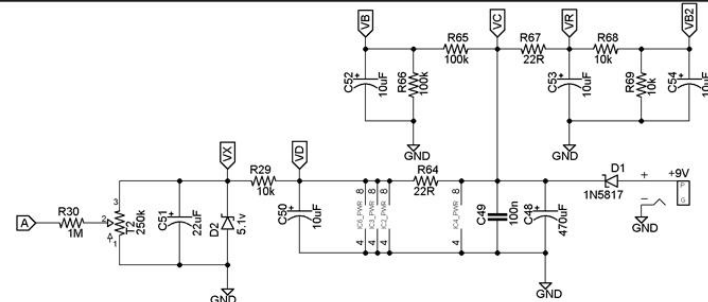

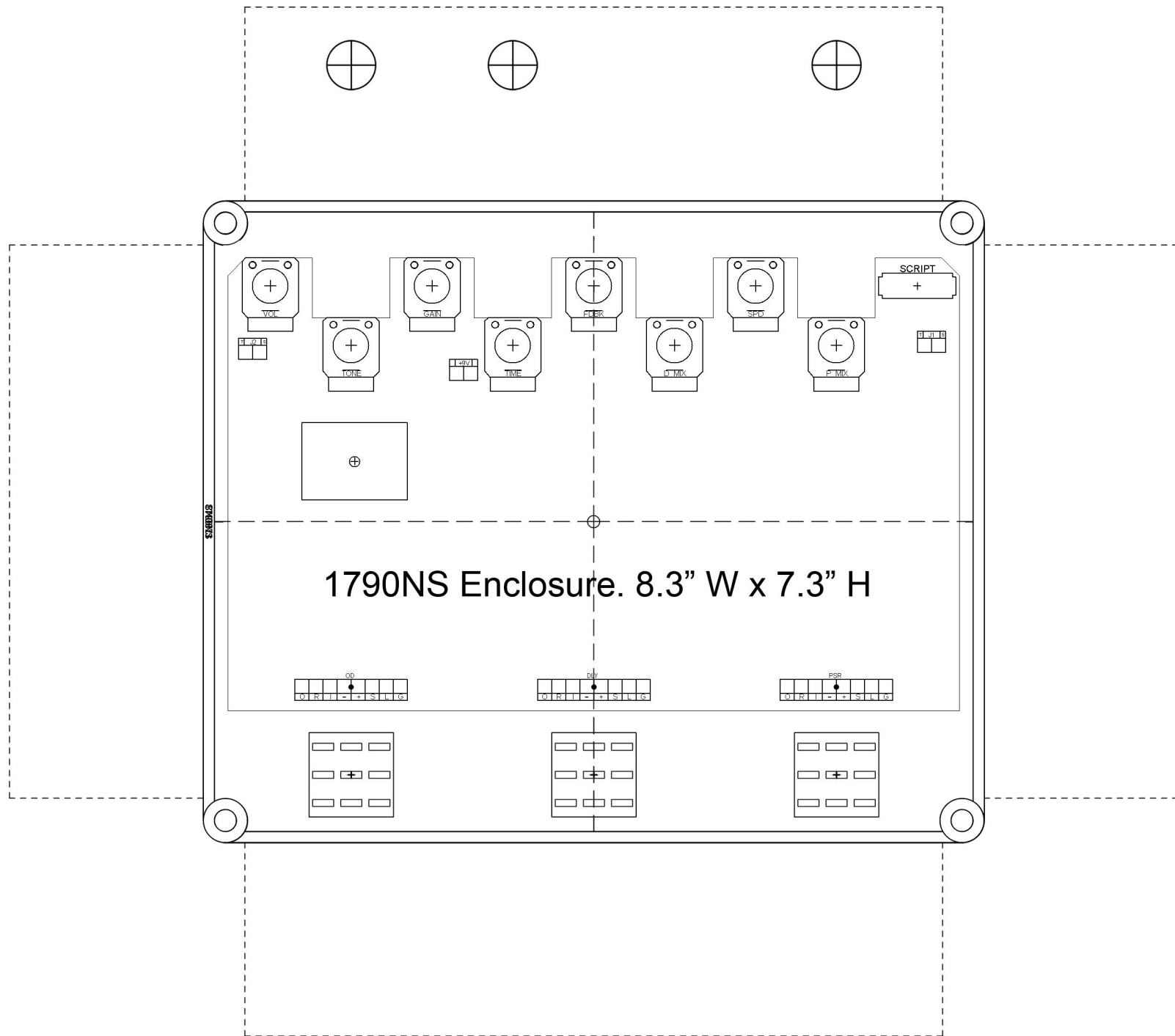

Overview

The **Laserwolf** is the first madbeanpedals multi-effect project. It is an attempt to replicate some of the coveted tones off the first few Van Halen albums. EVH famously used few effects straight into his Marshall amps to achieve what we all know as the “brown sound”. While I don’t claim the **Laserwolf** copies this sound exactly it will at least get you in the ballpark...probably the same inning, too!

The **Laserwolf** has three effect components: a phaser, a delay and an overdrive. The Phaser is a Phase 90 with a couple of extra mods. The delay is a standard PT2399-based delay voiced for degrading repeats. The overdrive is a mash-up of the BSIABII and the Wampler® Pinnacle™ (both being very similar).

The signal path can be altered via a 4PDT switch, as well. This offers the option of Phaser-Delay-Overdrive or Overdrive-Delay-Phaser (in series). Each effect can be turned on and off via the stomp switches. The reason for the order switching is that the Phaser-Delay-Overdrive option is most similar to how EVH used his effects; a Phase90 into an Echoplex into his amp. The second option, Overdrive-Delay-Phaser is closer to how guitar players arrange pedals on a pedalboard (overdrive before modulation or delay). Ideally, we might want a third option of Overdrive-Phaser-Delay but this would require yet another switch in an already complex build. However, the two existing options offer plenty of vareity and they do indeed sound different from one another.

Controls

OD Section: Vol, Tone and Gain.

Delay Section: Mix, Feedback and Delay.

Phaser Section: Speed, Mix and “Script”.

The OD and Delay controls are self-explanatory. The Feedback control on the delay will go into self-oscillation when turned up. You can modify where it does this by changing the value of R47. Lower values will result in earlier oscillation. A high enough value will prevent the delay from self-oscillating altogether.

The Phaser controls require explaining. The Speed control is obvious; down is slow and up is fast. You should use the C-Taper (reverse audio) listed. A B-taper will work but most of the speed changes will only happen in the last 1/3 of the rotation with it.

The Mix control is not standard. Fully counter-clockwise is the standard Phase 90 effect. As you turn the Mix control up, the effect slowly changes into vibrato instead of phase. The vibrato works best at medium speeds; too slow and you do not get much of an effect, and too fast the phase and vibrato sound pretty much the same.


Finally, the “Script” switch gives three options: two levels of phase feedback or no feedback (middle position). R19 and R74 set the amount of feedback level. I just picked what I liked in this circuit, but feel free to socket those resistors and play with them. Don’t go too low on the resistor values or you will just get a noisy mess. If you do not want feedback options, simply leave the switch off. Or, if you prefer just one feedback option use an On/On SPDT instead and leave R74 empty.

4PDT


The general lack of a small profile PCB-mounted 4PDT makes for a less than ideal combination of component footprints in the Laserwolf. The 4PDT toggle is really tall which causes the 9mm pots to hang further away from the enclosure when everything is soldered onto the PCB. It will require you to put a bit of pressure on the PCB to get the threads of the pots to clear the drill holes on your enclosure; not very much...just a little. I would avoid over-tightening the nuts on the pots to keep the pressure to a minimum. Finger-tight plus a little more should be enough to hold everything in place.

Alternatively, you could simply not push the 9mm pots all the way flush to the PCB to give them some extra height to match the 4PDT. A simple spacer underneath the pots when soldering would make this a relatively straight-forward task.

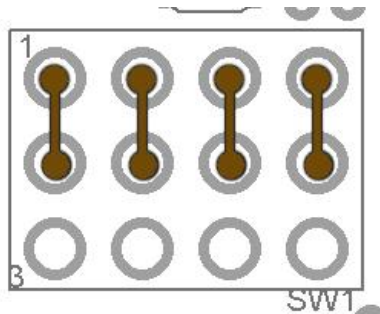You can omit the 4PDT if you do not want to have the order switching option by soldering jumpers between the middle row of pads to either of the outside rows.




Phaser-Delay-Overdrive (Up Position)

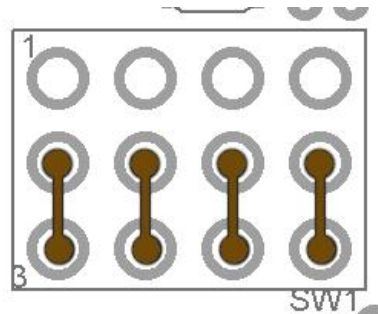

Overdrive-Delay-Phaser (Down Position)


Wiring

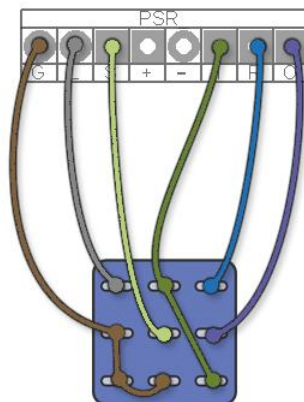Luckily, wiring the Laserwolf is incredibly easy!



This is the standard input-grounded scheme I use. You do not need to wire anything between the stomp switches, only to the bypass pads as shown. The + and – pads are for your indicator LED. These LEDs can be soldered directly to the PCB and do not require a bezel on the enclosure (unless you want one).

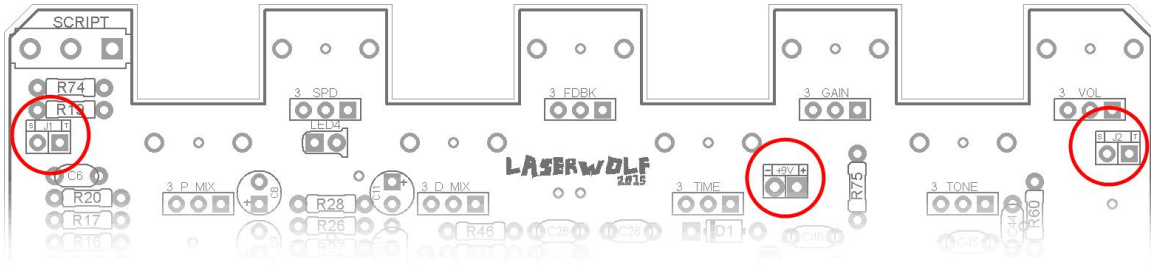Near the top of the PCB, J1 is wired to your INPUT jack. J2 goes to the OUTPUT jack. And the +9v and Ground pads go to your DC jack.



LED4 is the speed indicator for the Phaser effect. It can be soldered directly to the PCB, or left off entirely, if you like. Regarding LED4: I would socket R28 (the 560R resistor). This was used to “pull down” the LED on the bottom part of its swing to make the flashing more obvious. But, it can make the LED pretty unsymmetrical in its cycle. If you don’t like this, simply pull R28 from its socket.

Assembly Notes

Overdrive: There is one bias setting to perform. T1 sets the bias for the Q5 transistor. You can set this anywhere from 4.5 – 6.5v. I ended up with 6.5v on mine. You’ll see there is a “Bias” pad right next to Q5 for your DMM.

Mods:

More gain – lower R53 to 1k. Use J201 instead of 2n5457.
More volume output – lower R59 to 1k5.

C40 is a treble bleed cap on the Gain pot. Its stock value is 150pF. I did not like this on my build...it just felt thin and weak at low gain settings. So, I omitted it from my build. YMMV.

Delay: This is pretty much plug and play. You can manipulate the self-oscillation point by altering the value of R47 as I described earlier in the doc. You can increase the dry signal output by lowering the value of R34. You can increase the delay output by lowering the value of R48. The stock setting is about unity output on the dry signal and the delays are slightly louder than dry when the Mix knob is all the way up. You can increase the signal degradation of the repeats by changing R46 to 2k and C23 to 15n (like the Deep Blue Delay™).

Phaser: The phaser requires matched transistors for Q7, Q8, Q9 and Q10 to work properly. You can match these yourself or purchase matched sets from some online vendors. For info on who to match them, check out the documentation for the [Nom Nom project](#).

T2 sets the Vb bias for the phaser. It’s easy to dial in; just set the Speed control about half way up and adjust T2 until you get proper phasing. You can use different Speed settings to zone in on the optimal setting for T2.


Testing

Take your time. This is a very complicated build. The combination of many parts, switching and just the sheer size of it will make it one of the more challenging DIY projects you've attempted. The good news is if you follow all the instructions it will fire right up....mine worked the first time without any hassle. This is rare!

Since you are a thorough builder, I know you will be testing this thing out before wiring it all up and dropping it in an enclosure. I know this because you are a dedicated madbeaner and follow the "rock it before you box it" mantra like the religious doctrine it attempts to be. But, this project must be tested a little differently. You should check the functionality BEFORE soldering in the 4PDT switch. Once that switch is soldered in, you pretty much have to solder the stomp switches for it to work 100%. My suggestion is to assemble everything then wire up the +9v jack, and the S and R pads of each bypass. This is all you need to use on your testing rig. Connect the +9v/ground wires to your testing rig, then use the S (send) and R (return) wires on each effect to test them individually. Once you confirm each one is behaving, go ahead and solder that 4PDT and do the final assembly. As long as you follow the wiring instructions I do not think it is necessary to test it further before putting the entire rig in your enclosure (unless you really want to).

| Voltage readings from a 9.4v One Spot supply | | | | | | | | | |
|--|------|-----|------|-----|--------|-----|------|-----|------|
| IC5 | V | IC4 | V | IC2 | V | IC3 | V | IC6 | V |
| 1 | 4.98 | 1 | 4.56 | 1 | 4.13 | 1 | 4.13 | 1 | 4.13 |
| 2 | 2.5 | 2 | 4.56 | 2 | 4.13 | 2 | 4.13 | 2 | 4.13 |
| 3 | 0 | 3 | 4.54 | 3 | 3.94 | 3 | 4.13 | 3 | 4.13 |
| 4 | 0 | 4 | 0 | 4 | 0 | 4 | 0 | 4 | 0 |
| 5 | 2.82 | 5 | 4.54 | 5 | varies | 5 | 4.13 | 5 | 4.13 |
| 6 | 2.5 | 6 | 4.56 | 6 | varies | 6 | 4.13 | 6 | 4.13 |
| 7 | 0.61 | 7 | 4.57 | 7 | varies | 7 | 4.13 | 7 | 4.13 |
| 8 | 0.67 | 8 | 9.12 | 8 | 8.7 | 8 | 8.7 | 8 | 8.7 |
| 9 | 2.5 | | | | | | | | |
| 10 | 2.5 | | | | | | | | |
| 11 | 2.5 | | | | | | | | |
| 12 | 2.5 | | | | | | | | |
| 13 | 2.5 | | | | | | | | |
| 14 | 2.5 | | | | | | | | |
| 15 | 2.5 | | | | | | | | |
| 16 | 2.5 | | | | | | | | |

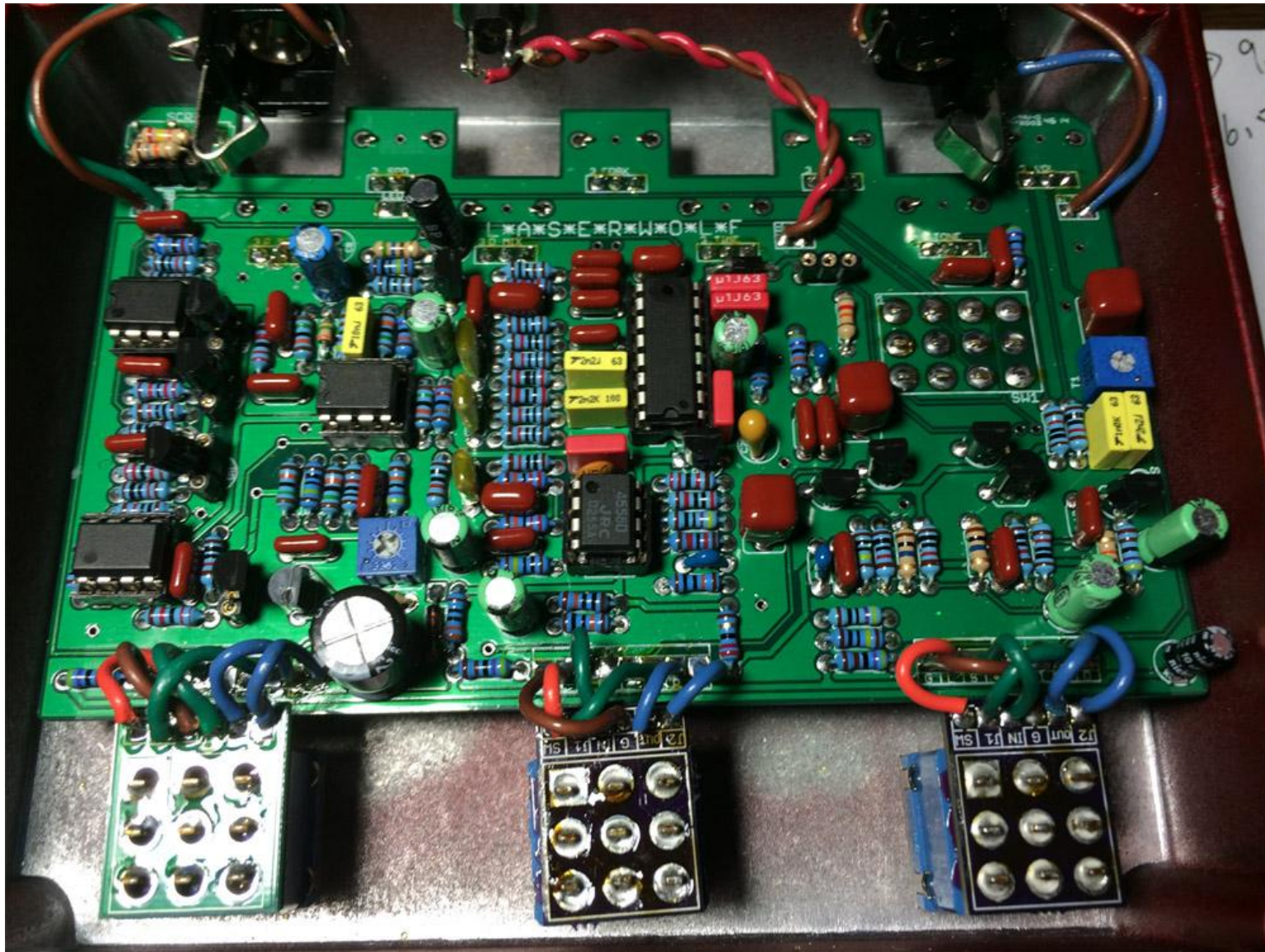Q5 set to 6.5v bias point. You can set this lower for more output (down to 4.5v)
Slight fluctuations on pin8 of IC2, IC3 and IC6, but seems to be okay.



Those are not cold joints on that stomp switch. I swear. Damn Kester solder...grumble grumble.